

# **DSD LAB REPORT**

## **LAB # 02**



**Spring 2021**

**CSE-308L Digital System Design Lab**

Submitted by: **ASHIQ ULLAH**

Registration No. : **18PWCSE1695**

Class Section: **B**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: \_\_\_\_\_

Submitted to:

**Engr. Madiha Sher**

April 24, 2021

Department of Computer Systems Engineering  
University of Engineering and Technology, Peshawar

## OBJECTIVES:

- Learn top down and bottom up design methodologies
- Data flow level modeling

## TASK01 (a):

Design 4-bit Ripple Carry Adder

1. First implement a Full adder using data gate level modeling.
2. Simulate the Full adder with a test bench.
3. Instantiate the Full adder four times and connect the circuit as shown.
4. Now again write a test bench and simulate the 4-bit RCA.

## CODE:

### Step1:

```
◆ In #  
1 module SUM(A, B, Cin, Sum);  
2     input A,B,Cin;  
3     output Sum;  
4     xor g0(Sum, A, B, Cin);  
5 endmodule  
6
```

```
◆ In #  
1 module CARRY(A, B, Cin, Cout);  
2     input A,B,Cin;  
3     output Cout;  
4     wire c1,c2,c3;  
5     and g0(c1, A, Cin);  
6     and g1(c2, B, Cin);  
7     and g2(c3, A, B);  
8     or g3(Cout, c1, c2, c3);  
9 endmodule  
10
```

```
◆ In #  
1 module FullAdder(A, B, Cin, Sum, Cout);  
2     input A,B,Cin;  
3     output Sum, Cout;  
4  
5     SUM S(A, B, Cin, Sum);  
6     CARRY C(A, B, Cin, Cout);  
7 endmodule  
8
```

**TestBench:**

### Step3:

```

1 module RCA(A, B, S, Cout);
2     input [0:3] A, B;
3     output [0:3] S;
4     output Cout;
5     wire [0:2] C;
6
7     FullAdder FA1(A[0], B[0], 0, S[0], C[0]);
8     FullAdder FA2(A[1], B[1], C[0], S[1], C[1]);
9     FullAdder FA3(A[2], B[2], C[1], S[2], C[2]);
10    FullAdder FA4(A[3], B[3], C[2], S[3], Cout);
11 endmodule
12

```

## Step4:

## TestBench:

```
1 module testB_RCA;
2     reg [3:0] A,B;
3     wire [3:0] S;
4     wire Cout;
5     RCA RCA1(A, B, S, Cout);
6     initial
7     begin
8
9         $display("          Decimal          |          Binary");
10        $display(" Num1 | Num2 | Carry | Sum |          Num1 | Num2 | Carry | Sum");
11        A[3] = 0; A[2] = 1; A[1] = 0; A[0] = 0;
12        B[3] = 1; B[2] = 0; B[1] = 1; B[0] = 0;
13        #5;
14        $monitor(" %d | %d | %d | %d | %b | %b | %b | %b",A,B,Cout,S,A,B,Cout,S);
15        #5;
16
17        A[3] = 0; A[2] = 1; A[1] = 1; A[0] = 0;
18        B[3] = 1; B[2] = 1; B[1] = 0; B[0] = 0;
19        #5;
20
21        A[3] = 0; A[2] = 1; A[1] = 0; A[0] = 1;
22        B[3] = 1; B[2] = 0; B[1] = 1; B[0] = 1;
23        #5;
24
25        A[3] = 0; A[2] = 0; A[1] = 1; A[0] = 1;
26        B[3] = 1; B[2] = 1; B[1] = 1; B[0] = 1;
27        #5;
28
29        A[3] = 0; A[2] = 0; A[1] = 0; A[0] = 1;
30        B[3] = 1; B[2] = 1; B[1] = 1; B[0] = 0;
31        #5;
32
33        A[3] = 0; A[2] = 1; A[1] = 1; A[0] = 1;
34        B[3] = 1; B[2] = 0; B[1] = 1; B[0] = 0;
35        #5;
36    end
37 endmodule
38
```


## OUTPUTS

## FULL ADDER:


## Truth Table:

#	A	B	Cin	Carry	Sum
# 0	0	0	0	0	0
# 1	0	0	1	0	1
# 2	0	1	0	0	1
# 3	0	1	1	1	0
# 4	1	0	0	0	1
# 5	1	0	1	1	0
# 6	1	1	0	1	0
# 7	1	1	1	1	1

## Circuit Design:

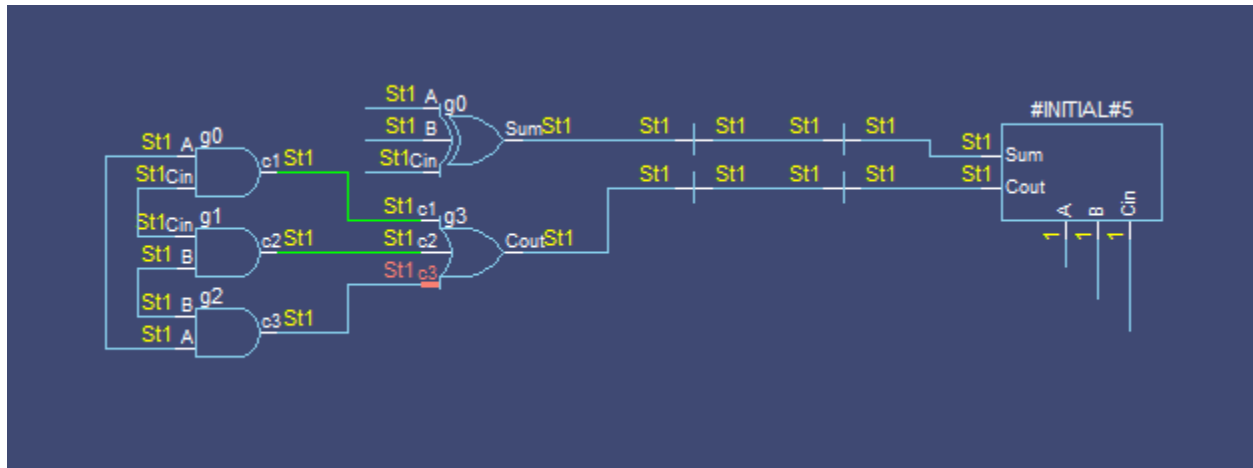

## Wave Form:

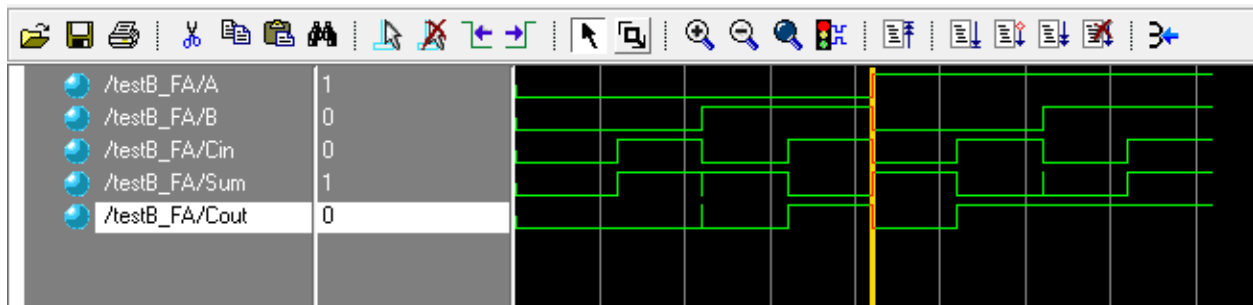


## RIPPLE CARRY ADDER:


### Truth Table:

#	Num1	Num2	Carry	Sum	Num1	Num2	Carry	Sum
#	4	10	0	14	0100	1010	0	1110
#	6	12	1	2	0110	1100	1	0010
#	5	11	1	0	0101	1011	1	0000
#	3	15	1	2	0011	1111	1	0010
#	1	14	0	15	0001	1110	0	1111
#	7	10	1	1	0111	1010	1	0001

## Circuit Design:

 

## Wave Form:

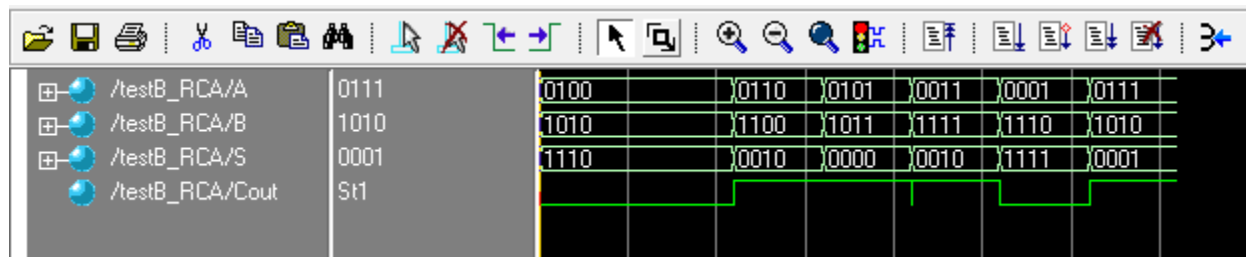

**TASK01 (b):**

Design the 4-bit full adder using data flow level modeling.

### Step1:

**CODE:**

```

1 module FA_DFlow(A, B, Cin, Sum, Cout);
2     input A,B,Cin;
3     output Sum, Cout;
4     wire c1,c2,c3;
5
6     assign Sum=(A ^ B ^ Cin);
7     assign c1=(A & B);
8     assign c2=(A & Cin);
9     assign c3=(B & Cin);
10    assign Cout=(c1 | c2 | c3);
11 endmodule
12

```

### Step2:

### TestBench:

```
E:/6TH SEMESTER/
```

```
1 module testB_FA_DFlow;
2     reg A,B,Cin;
3     wire Sum,Cout;
4     FA_DFlow FA6(A, B, Cin, Sum, Cout);
5     initial
6     begin
7         $display("\tA\t\t\tB\t\t\tCin\t\t\tCarry\t\t\tSum");
8         A = 0; B = 0; Cin = 0;
9         #1 $monitor("\t%b\t\t\t %b\t\t\t %b \t\t\t %b \t\t\t %b",A,B,Cin,Cout,Sum);
10        #5;
11
12        A = 0; B = 0; Cin = 1;
13        #5;
14        A = 0; B = 1; Cin = 0;
15        #5;
16
17        A = 0; B = 1; Cin = 1;
18        #5;
19        A = 1; B = 0; Cin = 0;
20        #5;
21
22        A = 1; B = 0; Cin = 1;
23        #5;
24        A = 1; B = 1; Cin = 0;
25        #5;
26        A = 1; B = 1; Cin = 1;
27        #5;
28    end
29 endmodule
```

### Step3:

```
1 module RCA_D(A, B, S, Cout);
2     input [3:0] A, B;
3     output [3:0] S;
4     output Cout;
5     wire [2:0] C;
6
7     FA_DFlow FA1(A[0], B[0], 1'b0, S[0], C[0]);
8     FA_DFlow FA2(A[1], B[1], C[0], S[1], C[1]);
9     FA_DFlow FA3(A[2], B[2], C[1], S[2], C[2]);
10    FA_DFlow FA4(A[3], B[3], C[2], S[3], Cout);
11 endmodule
12
```

### Step4:

#### TestBench:

```
1 module testB_RCA_D;
2     reg [3:0] A,B;
3     wire [3:0] S;
4     wire Cout;
5     RCA_D RCA1(A, B, S, Cout);
6     initial
7     begin
8         $display("          Decimal          |          Binary");
9         $display(" Num1 | Num2 | Carry | Sum |   Num1 | Num2 | Carry | Sum");
10        A[3] = 0; A[2] = 1; A[1] = 0; A[0] = 0;
11        B[3] = 1; B[2] = 0; B[1] = 1; B[0] = 0;
12        #5;
13        $monitor("%d | %d | %d | %d | %d | %d | %b | %b | %b | %b",A,B,Cout,S,A,B,Cout,S);
14        #5;
15
16        A[3] = 0; A[2] = 1; A[1] = 1; A[0] = 0;
17        B[3] = 1; B[2] = 1; B[1] = 0; B[0] = 0;
18        #5;
19
20        A[3] = 0; A[2] = 1; A[1] = 0; A[0] = 1;
21        B[3] = 1; B[2] = 0; B[1] = 1; B[0] = 1;
22        #5;
23
24        A[3] = 0; A[2] = 0; A[1] = 1; A[0] = 1;
25        B[3] = 1; B[2] = 1; B[1] = 1; B[0] = 1;
26        #5;
27
28        A[3] = 0; A[2] = 0; A[1] = 0; A[0] = 1;
29        B[3] = 1; B[2] = 1; B[1] = 1; B[0] = 0;
30        #5;
31
32        A[3] = 0; A[2] = 1; A[1] = 1; A[0] = 1;
33        B[3] = 1; B[2] = 0; B[1] = 1; B[0] = 0;
34        #5;
35
36    end
37 endmodule
38
39
```




OUTPUTS

Full Adder:


Truth Table:

#	A	B	Cin	Carry	Sum
#	0	0	0	0	0
#	0	0	1	0	1
#	0	1	0	0	1
#	0	1	1	1	0
#	1	0	0	0	1
#	1	0	1	1	0
#	1	1	0	1	0
#	1	1	1	1	1

Circuit Design:

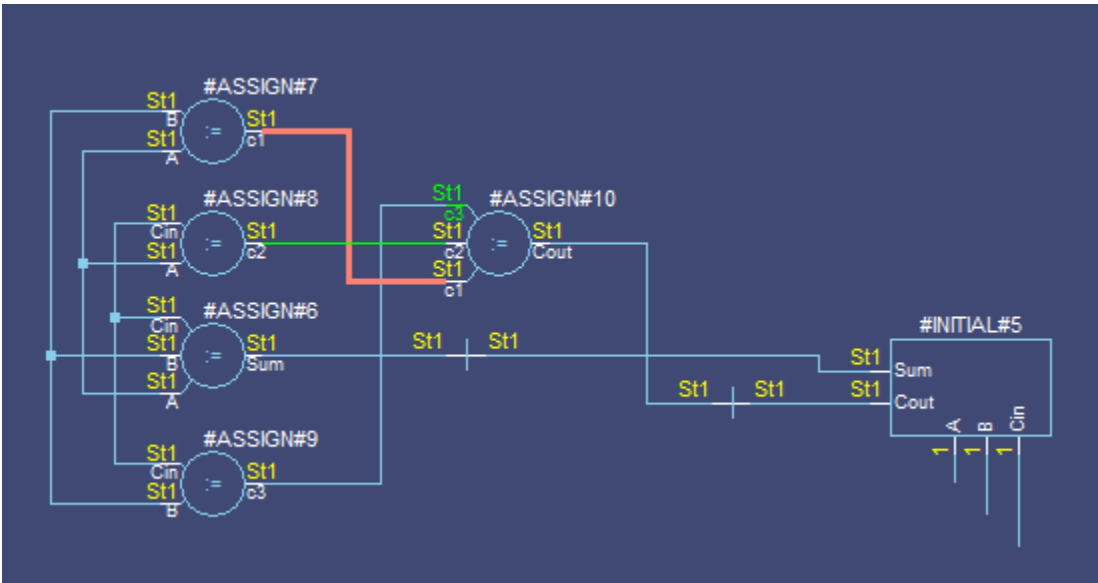

Wave Form:

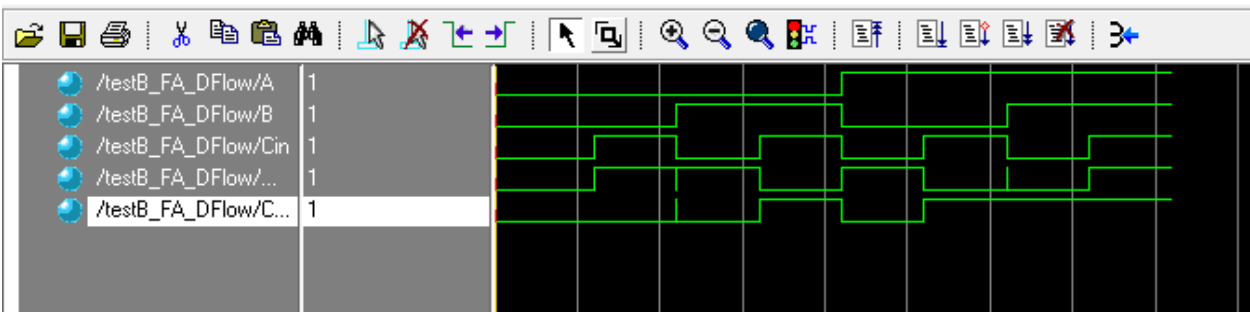


## Ripple Carry Adder:

### Truth Table:

#	Decimal				Binary			
#	Num1	Num2	Carry	Sum	Num1	Num2	Carry	Sum
#	4	10	0	14	0100	1010	0	1110
#	6	12	1	2	0110	1100	1	0010
#	5	11	1	0	0101	1011	1	0000
#	3	15	1	2	0011	1111	1	0010
#	1	14	0	15	0001	1110	0	1111
#	7	10	1	1	0111	1010	1	0001

### Circuit Design:

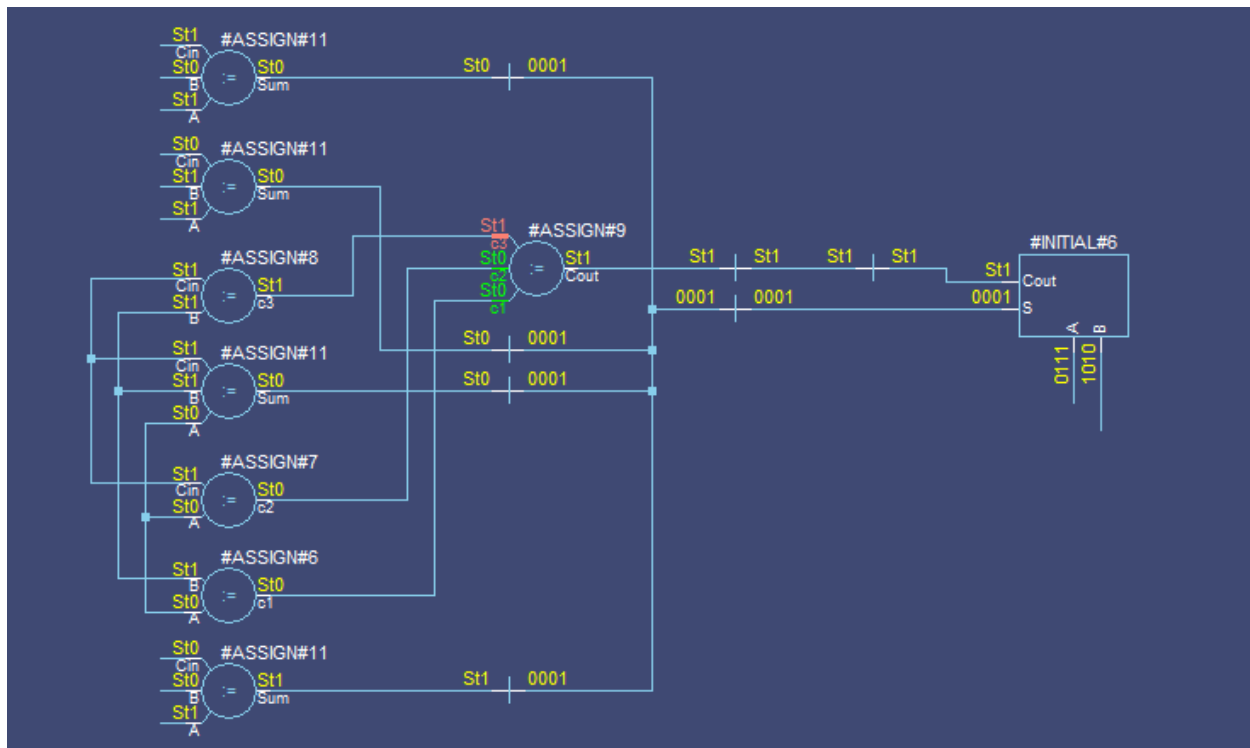

### Wave Form:

