

# FSM Lock Counter

Lab Report # 07



Spring 2020

CSE 308-L—Digital Systems Design--Lab

Submitted by: **Muhammad Asif Ayub**

Registration No: **17PWCSE1508**

Class Section: **A**

“On my honor, as student of Engineering and Technology, I have neither given nor received unauthorized assistance of this academic work”.

Submitted to:

**Engr. Madiha Sher**

Thursday, July 9, 2020<sup>th</sup>

# FSM Lock Counter

## Question 1:-

Build an electronic combination lock with reset button, two number buttons (0 and 1), and an unlock output. The combination should be “01011”.

 


Fig2: State Transition Diagram:

## Main Module:-

---

```
1 module FSM_UNLOCK_COUNTER (clk,reset,data0,data1,dataout);
2
3 input clk;
4 input reset,data0,data1;
5 reg [2:0]state;
6 reg [2:0]next_state;
7 output dataout;
8
9 parameter RESET = 0, state_0 = 1,
10             state_01 = 2, state_010 = 3,
11             state_0101 = 4, state_01011 = 5;
12
13 initial
14 begin
15     state <= RESET;
16     next_state <= RESET;
17 end
18
19 always @(posedge clk)
20 begin
21     state <= next_state;
22 end
23
24 always @(posedge clk or state or reset or data0 or data1)
25 begin
26     if(reset)
27         next_state <= RESET;
28     else
29         case(state)
30
31             RESET:    next_state <= data0 ? state_0 : data1 ? RESET : next_state;
32             state_0:  next_state <= data0 ? state_0 : data1 ? state_01 : next_state;
33             state_01: next_state <= data0 ? state_010 : data1 ? RESET : next_state;
34             state_010: next_state <= data0 ? state_0 : data1 ? state_0101 : next_state;
35             state_0101: next_state <= data0 ? state_010 : data1 ? state_01011 : next_state;
36             state_01011: next_state <= data0 ? state_0 : data1 ? RESET : next_state;
37             default:
38                 next_state <= RESET;
39         endcase
40 end
41 assign dataout = (next_state == state_01011);
42 endmodule
```

## Top Module:-

```
1 module FSM_TOP;
2
3 reg clk, reset,data0,data1;
4 wire dataout;
5
6 FSM_UNLOCK_COUNTER DUT (clk,reset,data0,data1,dataout);
7
8 initial
9 begin
10     clk=0;
11     reset=1;
12     data0 = 1;
13     data1 = 0;
14     #5 reset=0;
15     #10 data0 = 0;
16     data1 = 1;
17     #20 data0 = 1;
18     data1 = 0;
19     #30 data0 = 0;
20     data1 = 1;
21     #200 $finish;
22 end
23 always
24 #10 clk = ~clk;
25
26 initial
27 $monitor($time,":\t data0 = %d \t data1 = %d \t dataout=%d", data0, data1, dataout);
28
29 endmodule
```

```
# Compile of mainmodule.v was successful.
# Compile of topmodule.v was successful.
# 2 compiles. 0 failed with no errors.
vsim work.FSM_TOP
# vsim work.FSM_TOP
# Loading work.FSM_TOP
# Loading work.FSM_UNLOCK_COUNTER
run
#           0: data0 = 1  data1 = 0  dataout=0
#          15: data0 = 0  data1 = 1  dataout=0
#          35: data0 = 1  data1 = 0  dataout=0
#          65: data0 = 0  data1 = 1  dataout=0
#          70: data0 = 0  data1 = 1  dataout=1
#          90: data0 = 0  data1 = 1  dataout=0
# Compile of mainmodule.v was successful.
# Compile of topmodule.v was successful.
# 2 compiles. 0 failed with no errors.
quit -sim
```