

INTRODUCTION TO XILINX ISE AND S3BOARD

LAB # 01



Spring 2021

CSE-308L Digital System Design Lab

Submitted by: **ASHIQ ULLAH**

Registration No. : **18PWCSE1695**

Class Section: **B**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: _____

Submitted to:

Engr. Madiha Sher

April 17, 2021

Department of Computer Systems Engineering

University of Engineering and Technology, Peshawar

OBJECTIVES:

Introduction to FPGA and Xilinx

TASK01:

Develop a program to control on Board LED using On board available switch.

CODE:

```
1 module buffer(A0,A1,A2,A3,A4,A5,A6,A7,O1,O2,O3,O4,O5,O6,O7,O8);
2     input A0,A1,A2,A3,A4,A5,A6,A7;
3     output O1,O2,O3,O4,O5,O6,O7,O8;
4     buf b0(O1,A0);
5     buf b1(O2,A1);
6     buf b2(O3,A2);
7     buf b3(O4,A3);
8     buf b4(O5,A4);
9     buf b5(O6,A5);
10    buf b6(O7,A6);
11    buf b7(O8,A7);
12 endmodule
13
```

TestBench:


```
1 module test_buff;
2     reg A0,A1,A2,A3,A4,A5,A6,A7;
3     wire O1,O2,O3,O4,O5,O6,O7,O8;
4     buffer Buf1(A0,A1,A2,A3,A4,A5,A6,A7,O1,O2,O3,O4,O5,O6,O7,O8);
5     initial
6     begin
7         $display("      Inputs      |      Outputs");
8         A0 = 0; A1 = 0; A2 = 0; A3 = 0;
9         A4 = 0; A5 = 0; A6 = 0; A7 = 0;
10        #5;
11        $monitor ("%b %b %b %b %b %b %b %b | %b %b %b %b %b %b %b %b",A0,A1,A2,A3,A4,A5,A6,A7,O1,O2,O3,O4,O5,O6,O7,O8);
12        A0 = 0; A1 = 1; A2 = 0; A3 = 1;
13        A4 = 0; A5 = 1; A6 = 0; A7 = 1;
14        #5;
15
16        A0 = 0; A1 = 0; A2 = 1; A3 = 1;
17        A4 = 0; A5 = 0; A6 = 1; A7 = 1;
18        #5;
19
20        A0 = 1; A1 = 1; A2 = 0; A3 = 0;
21        A4 = 1; A5 = 1; A6 = 0; A7 = 0;
22        #5;
23
24        A0 = 0; A1 = 0; A2 = 1; A3 = 1;
25        A4 = 1; A5 = 1; A6 = 0; A7 = 0;
26        #5;
27
28        A0 = 1; A1 = 1; A2 = 0; A3 = 0;
29        A4 = 0; A5 = 0; A6 = 1; A7 = 1;
30        #5;
31
32        A0 = 1; A1 = 1; A2 = 1; A3 = 1;
33        A4 = 0; A5 = 0; A6 = 0; A7 = 0;
34        #5;
35
36        A0 = 0; A1 = 0; A2 = 0; A3 = 0;
37        A4 = 1; A5 = 1; A6 = 1; A7 = 1;
38        #5;
39
40        A0 = 1; A1 = 1; A2 = 1; A3 = 1;
41        A4 = 1; A5 = 1; A6 = 1; A7 = 1;
42        #5;
43    end
44 endmodule
45
```

OUTPUTS

Truth Table:

#	Inputs	Outputs
#0	1010101	101010101
#1	00110011	100110011
#2	11001100	11001100
#3	00111100	100111100
#4	11000011	110000011
#5	11110000	11110000
#6	00001111	100001111
#7	11111111	11111111

Circuit Design:

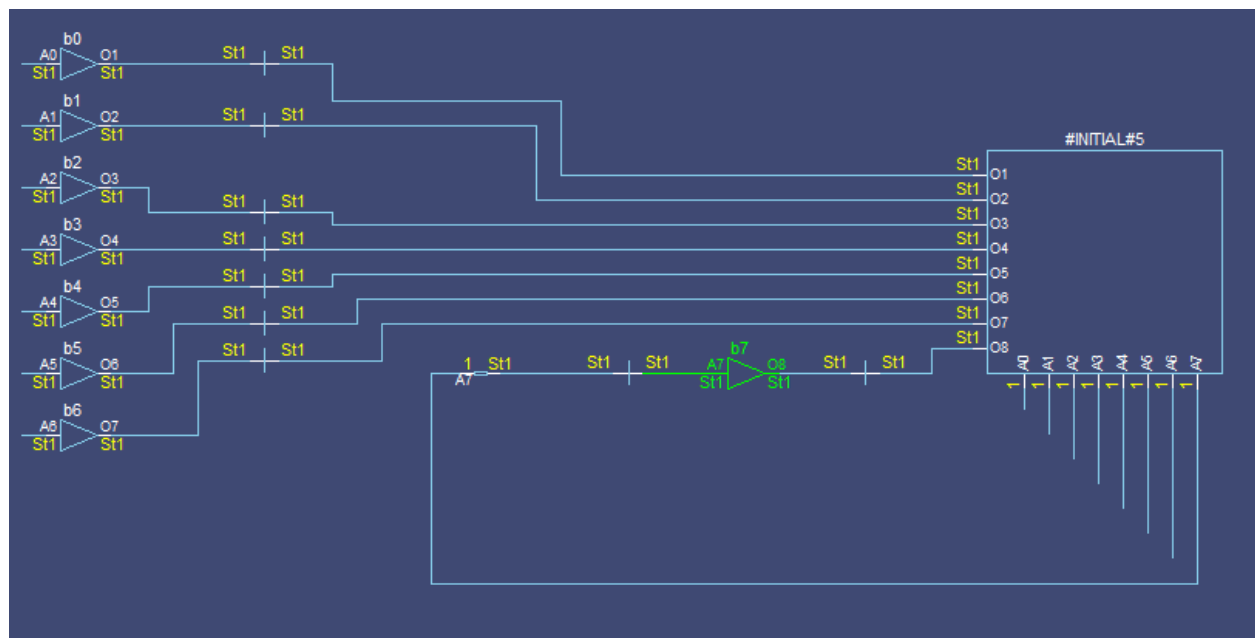

TASK02:

- a) Develop a program that implements a 2x1 multiplexer using gate level modeling.
 - i) Simulate the multiplexer with a test bench.

CODE:

Ln #
1 module mux_2tol(a,b,sel,f);
2 input a,b,sel;
3 output f;
4 wire nsel,f1,f2;
5 not g1(nsel,sel);
6 and g2(f1,a,nsel);
7 and g3(f2,b,sel);
8 or g4(f,f1,f2);
9 endmodule
10
11

TestBench:


Ln #	E:/6TH SEI
1 module test_2tol();	
2 reg a,b,sel;	
3 wire f;	
4 mux_2tol M(a,b,sel,f);	
5 initial	
6 begin	
7 \$display("A B SEL F");	
8 a=0;	
9 b=0;	
10 sel=0;	
11 \$monitor ("%b %b %b %b",a,b,sel,f);	
12 #5;	
13 a=0; b=0; sel=1;	
14 #5;	
15 a=0; b=1; sel=0;	
16 #5;	
17 a=0; b=1; sel=1;	
18 #5;	
19 a=1; b=0; sel=0;	
20 #5;	
21 a=1; b=0; sel=1;	
22 #5;	
23 a=1; b=1; sel=0;	
24 #5;	
25 a=1; b=1; sel=1;	
26 #5;	
27 a=1; b=1; sel=0;	
28 #5;	
29 a=1; b=1; sel=1;	
30 #5;	
31 a=1; b=1; sel=1;	
32 #5;	
33 end	
34 endmodule	
35	

OUTPUTS

Truth Table:

```
#A B S E L F
#0 0 0 0
#0 0 1 0
#0 1 0 0
#0 1 1 1
#1 0 0 1
#1 0 1 0
#1 1 0 1
#1 1 1 1
```

Circuit Design:

 

Wave:

/test_2to1/a	0
/test_2to1/b	0
/test_2to1/sel	0
/test_2to1/f	0

- b) Implement 4x1 mux using modelsim.
i) Simulate the multiplexer with a test bench.

CODE:

Ln #	
1	module mux_4to1(s1,s2,d3,d2,d1,d0,f);
2	input s1,s2,d3,d2,d1,d0;
3	output f;
4	wire ns1,ns2,a0,a1,a2,a3;
5	not n1(ns1,s1);
6	not n2(ns2,s2);
7	and g1(a0,ns1,ns2,d0);
8	and g2(a1,ns1,s2,d1);
9	and g3(a2,s1,ns2,d2);
10	and g4(a3,s1,s2,d3);
11	or o1(f,a0,a1,a2,a3);
12	endmodule

TestBench:

```
module test_4to1;

    reg s1,s2,d3,d2,d1,d0;

    wire f;

    mux_4to1 multi(s1,s2,d3,d2,d1,d0,f);

    initial
    begin

        $display("SEL1 SEL2 D3 D2 D1 D0 f");

        s1=0;

        s2=0;

        d3=0;d2=1;d1=0;d0=0;

        #1 $display("%b %b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);

        #5;

        s1=0;

        s2=0;
```

```

d3=0;d2=1;d1=0;d0=1;
#1 $display("%b %b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=0;
s2=0;
d3=0;d2=1;d1=1;d0=0;
#1 $display("%b %b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=0;
s2=0;
d3=0;d2=1;d1=1;d0=1;
#1 $display("%b %b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=0;
s2=1;
d3=1;d2=0;d1=0;d0=0;
#1 $display("%b %b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=0;
s2=1;
d3=1;d2=0;d1=0;d0=1;
#1 $display("%b %b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=0;
s2=1;
d3=1;d2=0;d1=1;d0=0;
#1 $display("%b %b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;

```

```

s1=0;
s2=1;
d3=1;d2=0;d1=1;d0=1;
#1 $display("%b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=1;
s2=0;
d3=1;d2=0;d1=1;d0=1;
#1 $display("%b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=1;
s2=0;
d3=1;d2=0;d1=0;d0=0;
#1 $display("%b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=1;
s2=0;
d3=1;d2=1;d1=0;d0=1;
#1 $display("%b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=1;
s2=0;
d3=1;d2=1;d1=1;d0=0;
#1 $display("%b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=1;
s2=1;
d3=0;d2=1;d1=0;d0=1;

```



```

#1 $display("%b %b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=1;
s2=1;
d3=1;d2=1;d1=1;d0=0;
#1 $display("%b %b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;
s1=1;
s2=1;
d3=1;d2=1;d1=1;d0=1;
#1 $display("%b %b %b %b %b %b %b",s1,s2,d3,d2,d1,d0,f);
#5;

end
endmodule

```

OUTPUTS


Truth Table:

```

# SEL1 SEL2 D3 D2 D1 D0 f
# 0001000
# 0001011
# 0001100
# 0001111
# 0110000
# 0110010
# 0110101
# 0110111
# 1010110
# 1010000
# 1011011
# 1011101
# 1101010
# 1111101
# 1111111

```

Circuit Design:

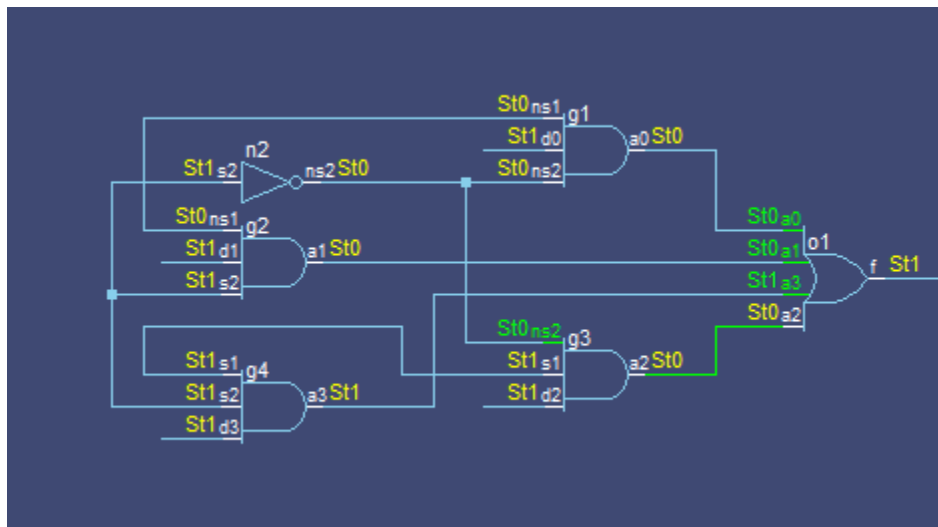

Wave:

