 


LAB # 10



Spring 2021

CSE-308L Digital System Design Lab

Submitted by: Hurair Mohammad

Registration No. : 18PWCSE1657

Class Section: B

"On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work."

Student Signature: _____

Submitted to:

Engr. Madiha Sher

**Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar**

MODULE

```
module traffic_light(light_highway, light_farm, C, clk, rst_n); parameter
HGRE_FRED=2'b00,HYEL_FRED =
3'b001,HRED_FGRE=3'b010,HRED_FYEL=3'b100; input C,clk,rst_n;
output reg[2:0] light_highway, light_farm; reg[27:0] count=0,count_delay=0;
reg delay10s=0,
delay3s1=0,delay3s2=0,RED_count_en=0,YELLOW_count_en1=0,YELLOW_
count_e n2=0; wire clk_enable; reg[1:0] state, next_state; always @(posedge
clk or negedge rst_n) begin if(~rst_n) state <= 3'b001; else
state <= next_state; end always @(*) begin case(state)
HGRE_FRED: begin // Green on highway and red on farm way
RED_count_en=0;
YELLOW_count_en1=0; YELLOW_count_en2=0; light_highway = 3'b001;
light_farm = 3'b100; if(C) next_state = HYEL_FRED; else next_state
=HGRE_FRED;
end
HYEL_FRED: begin light_highway = 3'b010; light_farm = 3'b100;
RED_count_en=0;
YELLOW_count_en1=1; YELLOW_count_en2=0;
if(delay3s1) next_state = HRED_FGRE; else next_state = HYEL_FRED;
end
HRED_FGRE: begin light_highway = 3'b100; light_farm = 3'b001;
RED_count_en=1;
YELLOW_count_en1=0; YELLOW_count_en2=0;
if(delay10s) next_state = HRED_FYEL;
// red in 10s then turn to yello -> green again for high way else next_state
=HRED_FGRE;
end
HRED_FYEL:begin// red on highway and yellow on farm way light_highway =
3'b100; light_farm = 3'b010; RED_count_en=0;
YELLOW_count_en1=0; YELLOW_count_en2=1;
if(delay3s2) next_state = HGRE_FRED; else next_state =HRED_FYEL; end
default: next_state = HGRE_FRED; endcase end
always @(posedge clk) begin
if(clk_enable==1) begin
if(RED_count_en||YELLOW_count_en1||YELLOW_count_en2)
count_delay <=count_delay + 1; if((count_delay == 9)&&RED_count_en)
begin delay10s=1; delay3s1=0; delay3s2=0; count_delay<=0; end
else if((count_delay == 2)&&YELLOW_count_en1) begin delay10s=0;
delay3s1=1; delay3s2=0; count_delay<=0; end
else if((count_delay == 2)&&YELLOW_count_en2) begin delay10s=0;
delay3s1=0; delay3s2=1; count_delay<=0; end else begin
delay10s=0; delay3s1=0; delay3s2=0; end end end
always @(posedge clk) begin
count <=count + 1; if(count == 50000000) if(count == 3) count <= 0; end
```

```
    assign clk_enable = count==3 ? 1: 0;
endmodule
```

```
/////////////////////////////////////////////////////////////////
net "clk" loc = V10 | iostandard = LVCMOS33 | PERIOD = 50MHZ; net "rst_n"
loc = M18 | iostandard = LVCMOS33 | DRIVE = 8 | SLEW = FAST | PULLUP;
net "C" loc = F17 | iostandard = LVCMOS33 | DRIVE = 8 | SLEW = FAST |
PULLUP;
net "light_highway[0]" loc = P15 | iostandard = LVCMOS33 | DRIVE = 8 |
SLEW = FAST;
net "light_highway[1]" loc = P16 | iostandard = LVCMOS33 | DRIVE = 8 |
SLEW = FAST;
net "light_highway[2]" loc = N15 | iostandard = LVCMOS33 | DRIVE = 8 |
SLEW = FAST;
net "light_farm[0]" loc = N16 | iostandard = LVCMOS33 | DRIVE = 8 | SLEW =
FAST;
net "light_farm[1]" loc = U17 | iostandard = LVCMOS33 | DRIVE = 8 | SLEW =
FAST;
net "light_farm[2]" loc = U18 | iostandard = LVCMOS33 | DRIVE = 8 | SLEW =
FAST;
```